

Test Tuesday 5/15

- Electrostatics
- Circuits

Electric field equation:

$$E = \frac{k|q|}{r^2}$$

this equation gives the magnitude
of the electric field

direction comes from arrows of
the electric field

- if there are multiple charges,
we must calculate electric field
from each.


Resistors:

- The point of resistors is to control current
- Two ways to connect pieces:

1. Series



2. Parallel

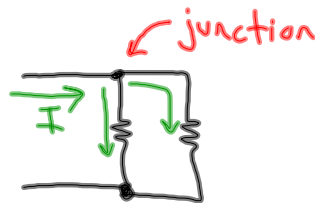

- There is a relationship between current, voltage, and resistance:


$$V = IR$$

$$\text{voltage} = (\text{current})(\text{resistance})$$

Ohm's law


- Equivalent resistance:

- Series

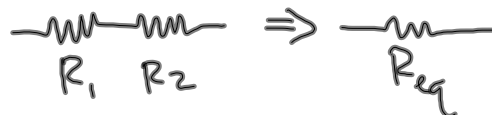


$$R_{eq} = R_1 + R_2$$

- Parallel

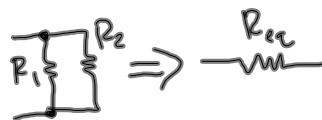


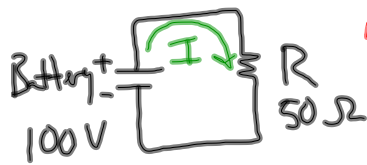
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$



Assume wire do not have any resistance

$$V = IR$$
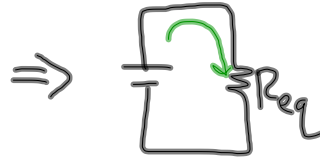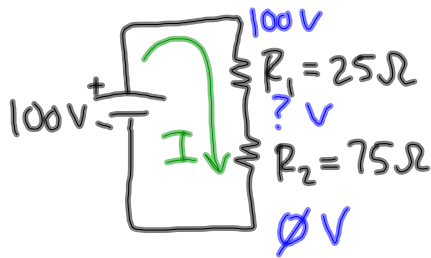
$$I = \frac{V}{R} = \frac{100\text{ V}}{50\Omega} = 2\text{ A}$$



$$R_{eq} = R_1 + R_2 = 100\Omega$$

Pieces in series share current.

They have different voltage drops.

$$I_{\text{total}} = \frac{V_{\text{battery}}}{R_{eq}} = \frac{100\text{ V}}{100\Omega} = 1\text{ A}$$

$$V_1 = I_{\text{total}} R_1 = (1\text{ A})(25\Omega) = 25\text{ V}$$

amount of voltage each resistor is using.

$$V_2 = I_{\text{total}} R_2 = (1\text{ A})(75\Omega) = 75\text{ V}$$



"voltage drop"

$$V_1 + V_2 = V_{\text{battery}}$$

$$25\text{ V} + 75\text{ V} = 100\text{ V} \quad \checkmark$$

All voltage drops must add

to the battery voltage

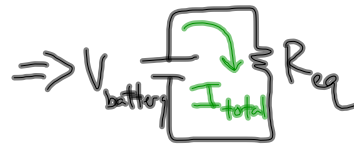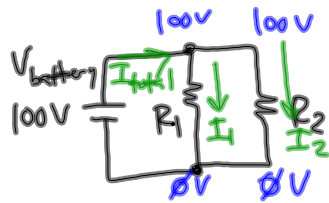

$$R_1 = 25 \Omega$$

$$R_2 = 75 \Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$R_{eq} = \left[\frac{1}{25 \Omega} + \frac{1}{75 \Omega} \right]^{-1}$$

$$\text{calculator: } \left(\left(\frac{1}{25} \right) + \left(\frac{1}{75} \right) \right)^{-1}$$

$$R_{eq} = 18.75 \Omega$$

$$I_{total} = \frac{V_{battery}}{R_{eq}} = \frac{100 \text{ V}}{18.75 \Omega} = 5.33 \text{ A}$$

Pieces in parallel share voltage.

They have different currents.

$$I_1 = \frac{V_{battery}}{R_1} = \frac{100 \text{ V}}{25 \Omega} = 4 \text{ A}$$


$$I_2 = \frac{V_{battery}}{R_2} = \frac{100 \text{ V}}{75 \Omega} = 1.33 \text{ A}$$

$$I_1 + I_2 = I_{total}$$


$$4 \text{ A} + 1.33 \text{ A} = 5.33 \text{ A} \checkmark$$

Current in each branch must equal the total current coming into the branch

Equivalent Resistance Practice:

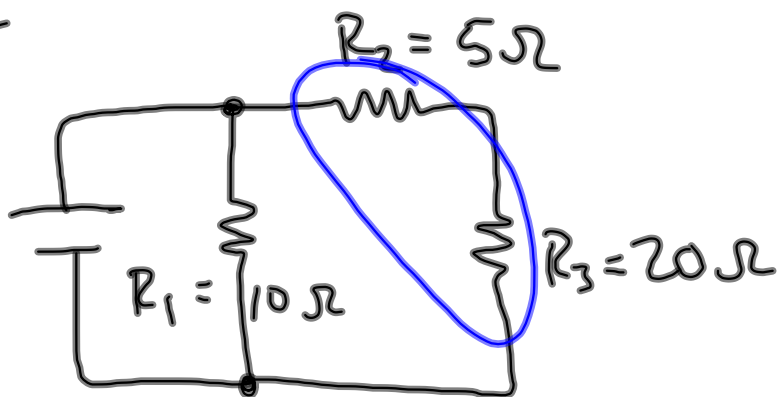


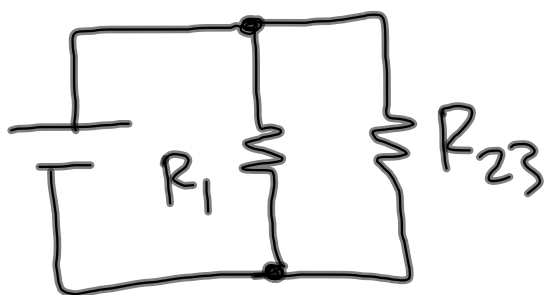Start with resistor that is farthest from battery and work towards the battery





$$R_{23} = R_2 + R_3$$

$$= 25\ \Omega$$

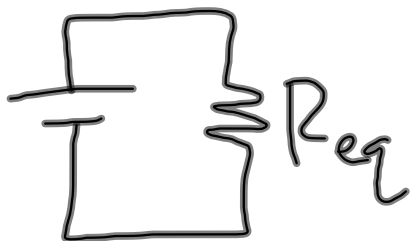


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_{23}}$$

$$R_{eq} = 7.14\ \Omega$$

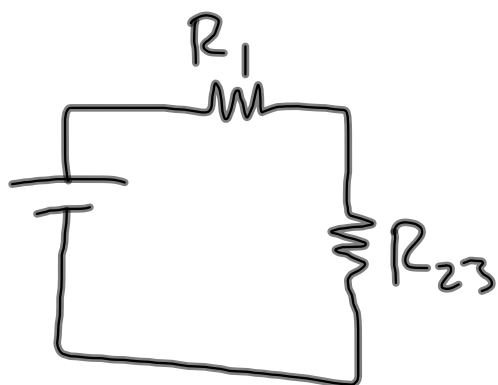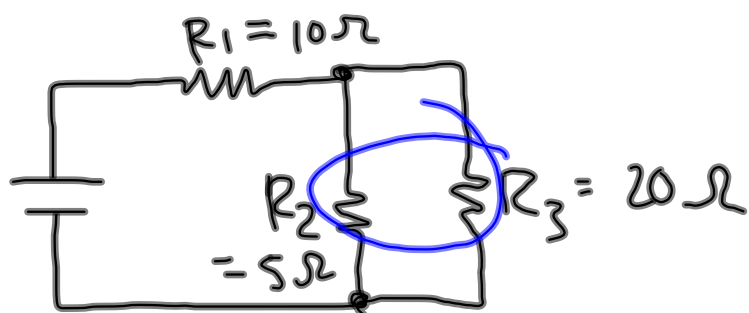

$$\frac{1}{R_{23}} = \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{23} = 4\Omega$$

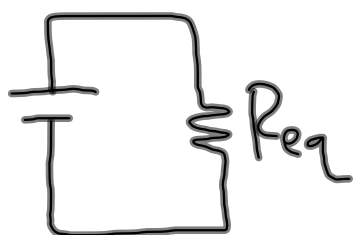

$$R_{eq} = R_1 + R_{23}$$

$$= 14\Omega$$

Electric Power:

$$P = IV$$

Units are still Watts

$$P = I^2 R = \frac{V^2}{R}$$